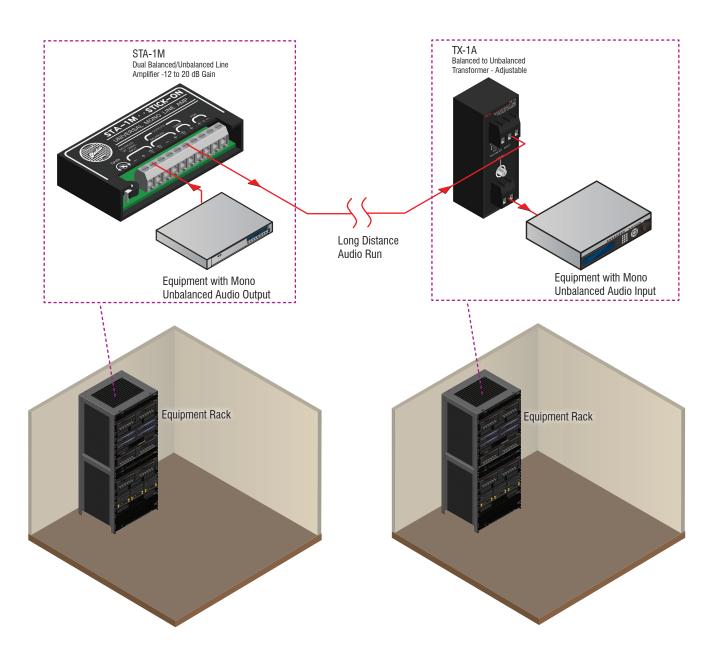
MONO AUDIO FORMAT CONVERSION
Balanced Audio Amplification for a Long Cable Run Connecting Unbalanced Equipment





## Description:

The STA-1M Mono Line Amplifier is used to balance an unbalanced signal and amplify it to  $\pm 4$  dBu balanced for a long cable run. The TX-1A at the receiving end provides transformer isolation, adjustable attenuation and format conversion to match the unbalanced equipment input.

Note: The STA-1M input may be wired for balanced or unbalanced operation.



Parts List Product QTY STA-1M TX-1A

Recommended Pwr. Supplies **Product** QTY PS-24AS 24 Vdc 500 mA

